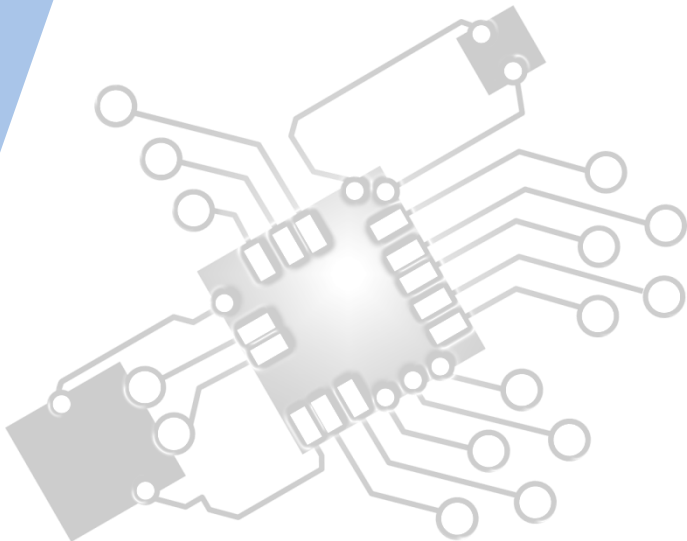




Computer Organisation


IB Computer Science



Content developed by
Dartford Grammar School
Computer Science Department



HL Topics 1-7, D1-4

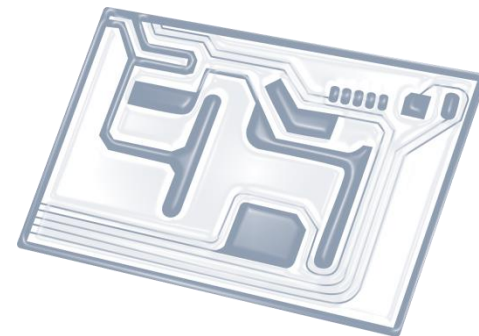

1: System design



2: Computer Organisation



3: Networks



4: Computational thinking



5: Abstract data structures



6: Resource management



7: Control



D: OOP

HL & SL 2 Overview

Computer architecture

2.1.1 Outline the architecture of the central processing unit (CPU) and the functions of the arithmetic logic unit (ALU) and the control unit (CU) and the registers within the CPU

2.1.2 Describe primary memory. 2 Distinguish between random access memory (RAM) and read-only memory (ROM), and their use in primary memory

2.1.3 Explain the use of cache memory

2.1.4 Explain the machine instruction cycle

Secondary memory

2.1.5 Identify the need for persistent storage

Operating systems and application systems

2.1.6 Describe the main functions of an operating system

2.1.7 Outline the use of a range of application software

2.1.8 Identify common features of applications

Binary representation

2.1.9 Define the terms: bit, byte, binary, denary/decimal, hexadecimal

2.1.10 Outline the way in which data is represented in the computer

Simple logic gates

2.1.11 Define the Boolean operators: AND, OR, NOT, NAND, NOR and XOR

2.1.12 Construct truth tables using the above operators

2.1.13 Construct a logic diagram using AND, OR, NOT, NAND, NOR and XOR gates



1: System design

2: Computer Organisation



3: Networks

4: Computational thinking



5: Abstract data structures


6: Resource management



7: Control


D: OOP



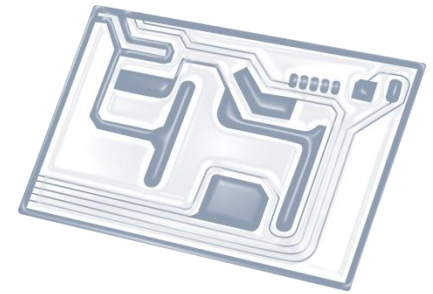


Topic 2.1.11

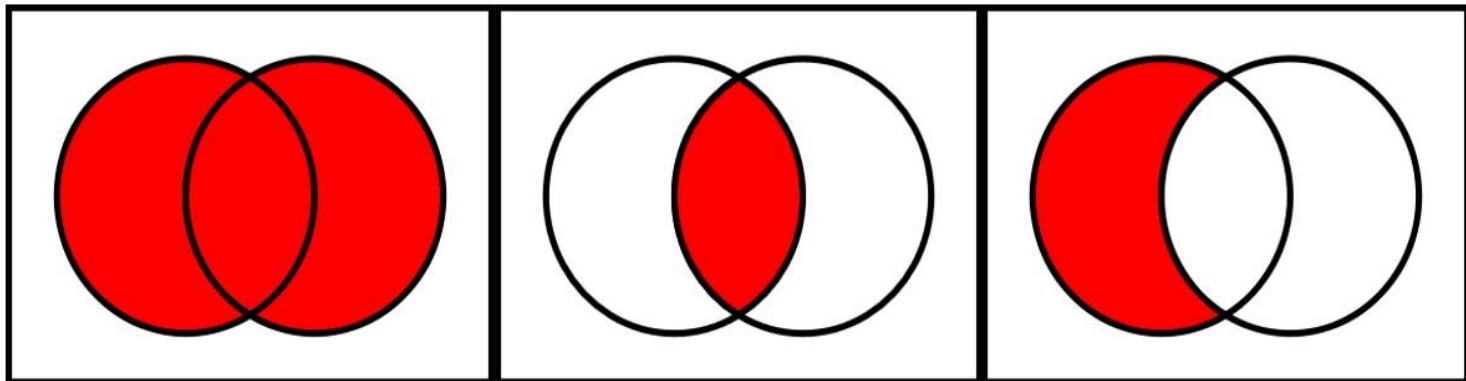Define the Boolean operators: **AND**, **OR**, **NOT**, **NAND**, **NOR** and **XOR**






What is logic?

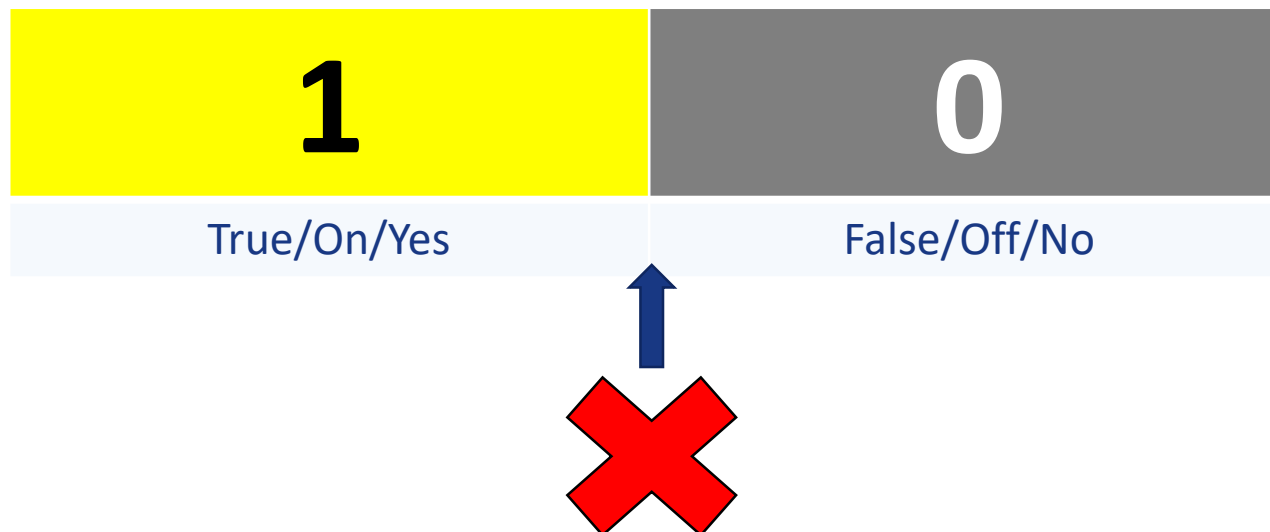- Its how a machine will solve problems.
- Machines (at basic level) do not understand semantics like humans – no grey areas.



The Basic 3 gates

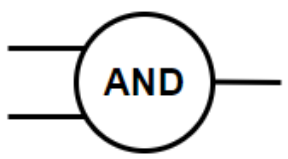
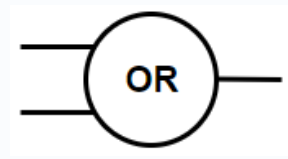
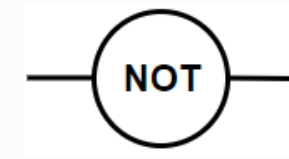
AND	OR	NOT
		

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

INPUT		OUTPUT
A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

INPUT	OUTPUT
A	NOT A
0	1
1	0

The Next 3 gates

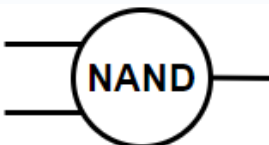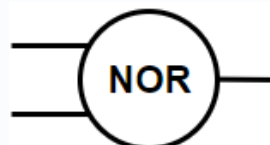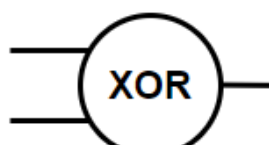NAND	NOR	XOR
		

INPUT		OUTPUT
A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0



INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0




Exam note!

The IB uses their **own symbols** for logic gates, not the British Standard ones you'll find on the web.

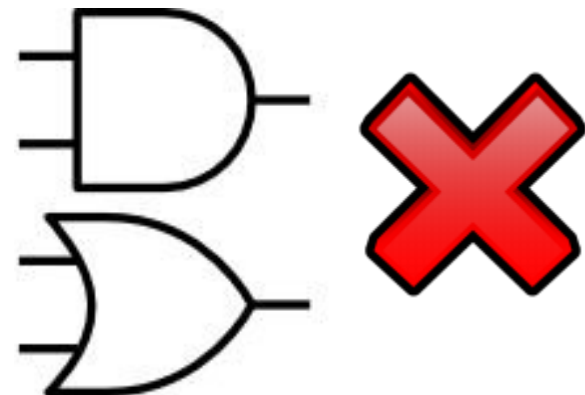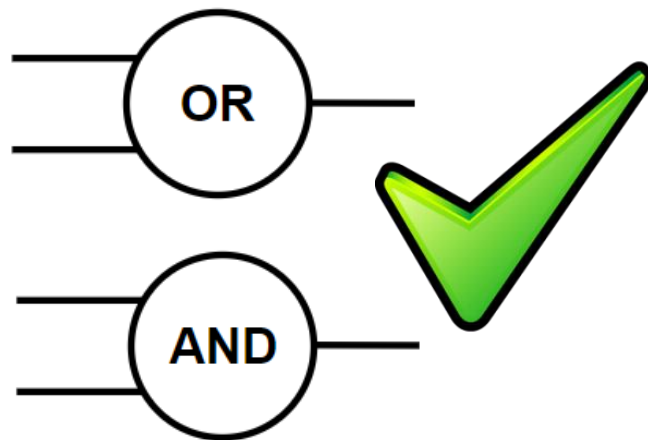All exams & mark schemes will only ever contain the ones highlighted in the official pseudo code guidance booklet




Combining gates (example 1)

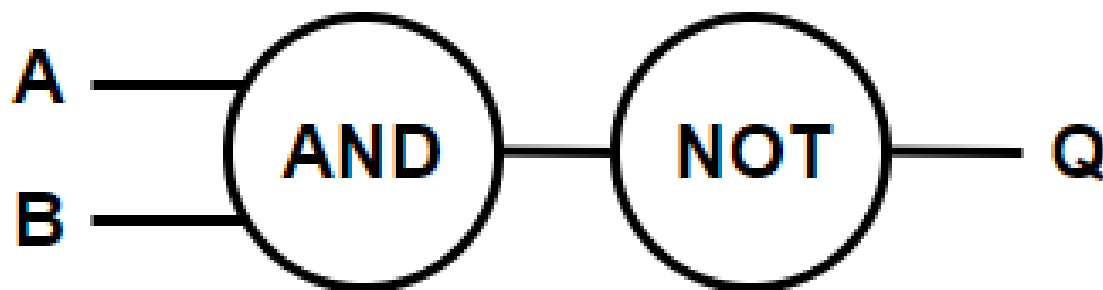

$$Q = \text{NOT } (A \text{ AND } B)$$

Can also be written as: $(A \cap B)'$


Combining gates (example 2)

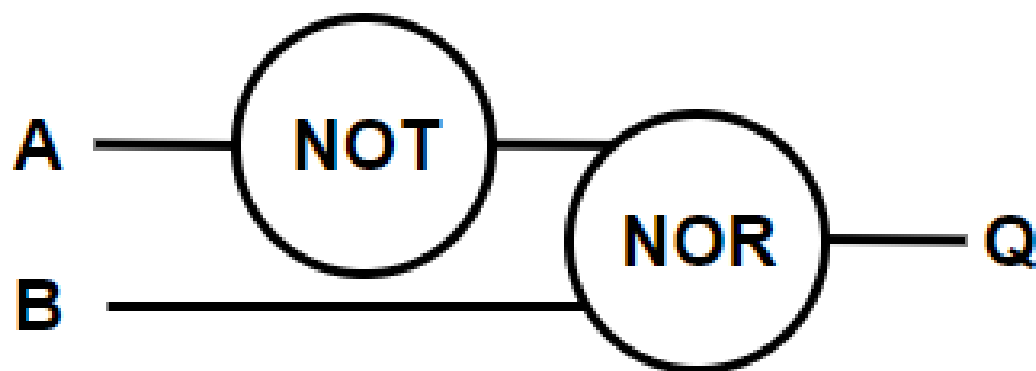

$$Q = \text{NOT } A \text{ NOR } B$$

Can also be written as: $\neg A \bar{\vee} B$

Combining gates (example 3)

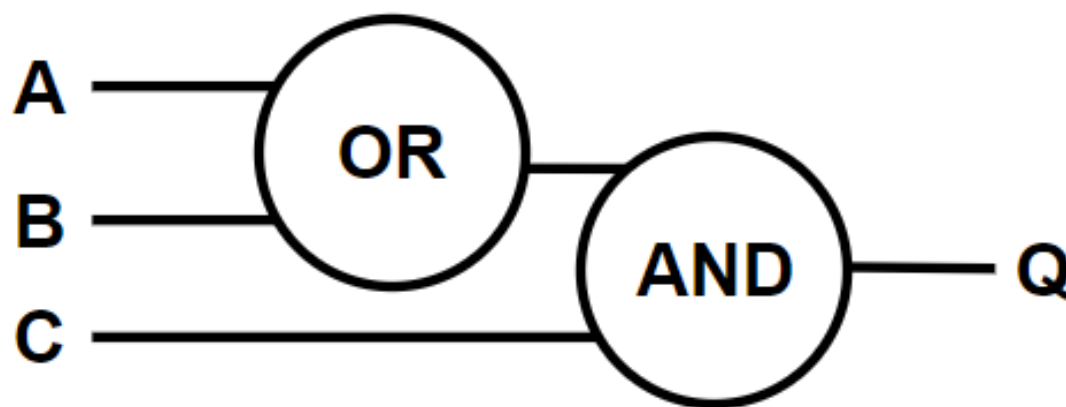

$$Q = C \text{ AND } (A \text{ OR } B)$$

Can also be written as: $C \wedge (A \vee B)$

Useful tool: **Wolfram Alpha**

Wolfram Alpha Boolean Algebra Calculator

Boolean Algebra Calculator

Enter the statement:

[Use AND, OR, NOT, XOR, NAND, NOR, and XNOR, IMPLIES and parentheses]

Submit

Input:

$$C \wedge (A \vee B)$$

$$C \text{ AND } (A \text{ OR } B)$$

Truth table:

C	A	B	$C \wedge (A \vee B)$
T	T	T	T
T	T	F	F
T	F	T	T
T	F	F	F
F	T	T	F
F	T	F	F
F	F	T	F
F	F	F	F

Also does truth tables!

Reality check

Where can we find these gates in the real world?



Possible **real-world** applications

Gate	Example
AND	Fire alarm: Smoke (1) AND heat (1)
OR	Internal car light: Either door open (1)
NOT	Microwave will stop (0) if the door is open (1). Vice versa....
NAND	Security system is engaged up until both the correct code and ID are scanned, then it disengages.
NOR	Air conditioning: AC will only come on (1) if BOTH windows A and B are closed. (0)
XOR	2 light switches in one corridor